

**COURSE: UCS1502 - MICROPROCESSORS AND INTERFACING**

## **Timer Interface – 8253/8254**

S. Angel Deborah  
Assistant Professor, Dept. of CSE




# Learning Objective

- To understand the architecture of 8253/8254
- To understand 8253's operation


# Overview

- Pin diagram of 8253
- Architecture
- Control word
- Modes of operation

# 8253 Pin Diagram

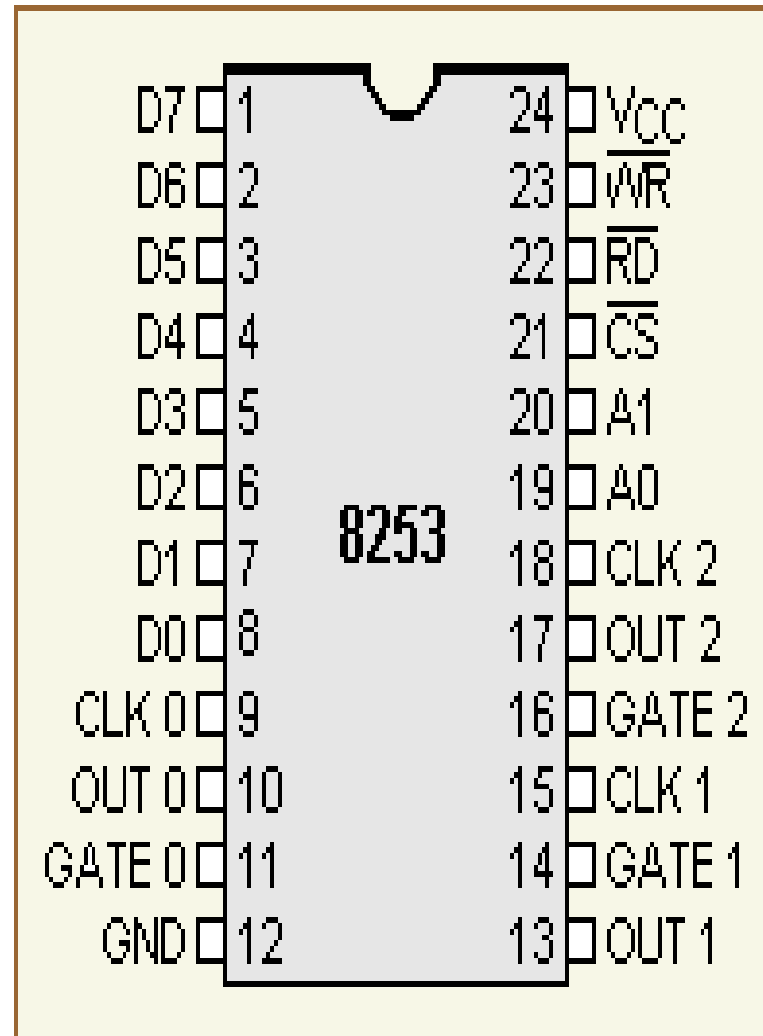

# 8253 Block Diagram

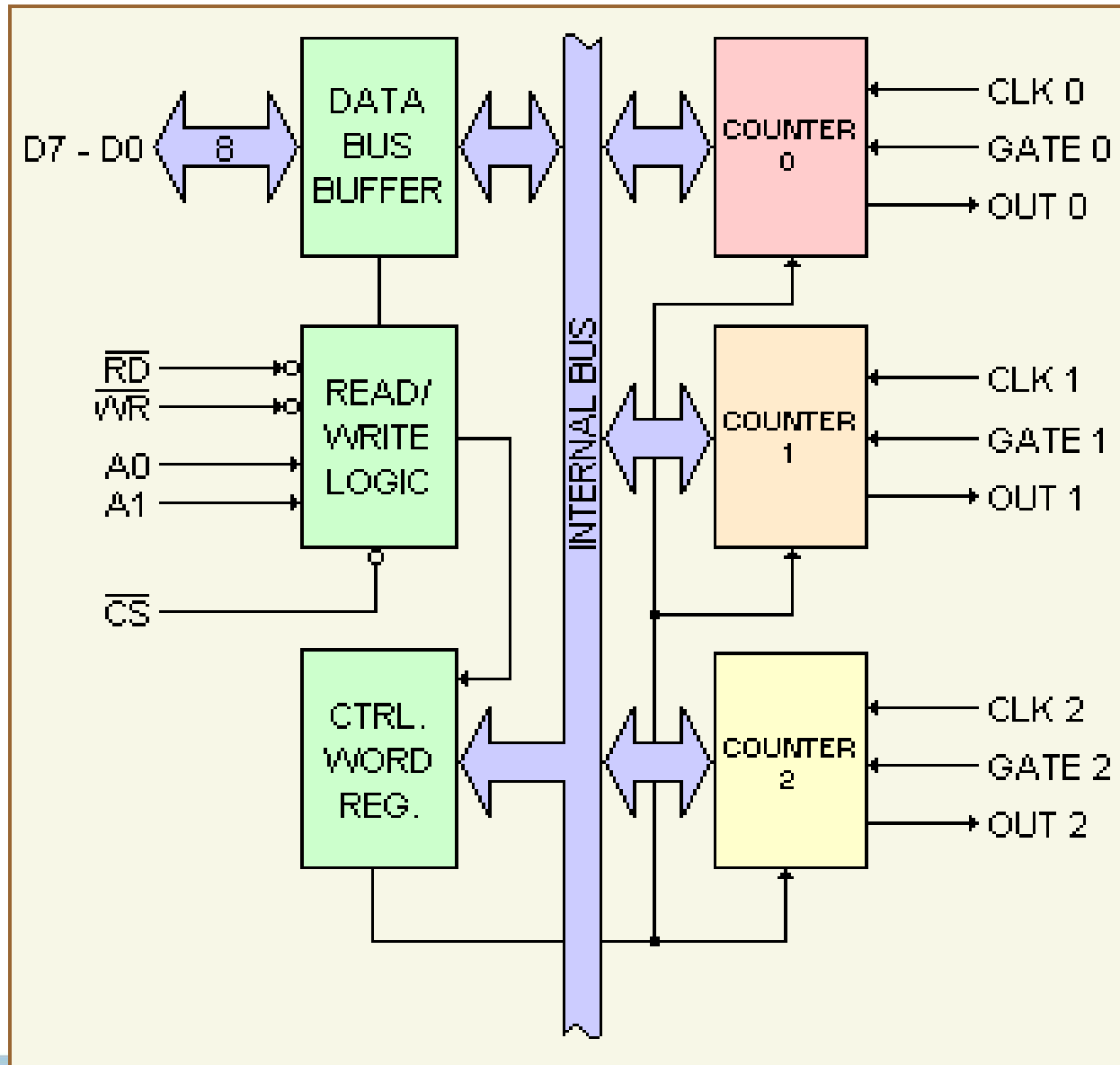

# Pin Description

- **Clock:** This is the clock input for the counter. The counter is 16 bits.
  - The maximum clock frequency is 1 / 380 nanoseconds or 2.6 megahertz. The minimum clock frequency is DC or static operation.
- **Out:** This single output line is the signal that is the final programmed output of the device.
  - Actual operation of the out line depends on how the device has been programmed.
- **Gate:** This input can act as a gate for the clock input line, or it can act as a start pulse, depending on the programmed mode of the counter.



# Counter Features

- Each counter is **identical**, and each consists of a **16-bit**, pre-settable, **down** counter.
- Each is **fully independent** and can be easily read by the CPU.
- When the counter is read, the data within the counter **will not be disturbed**.
- This allows the system or your own program to **monitor** the counter's value at any time, without disrupting the overall function of the 8253.

# Counter Selection

	$\overline{RD}$	$\overline{WR}$	A0	A1	function
COUNTER 0	1	0	0	0	Load counter 0
	0	1	0	0	Read counter 0
COUNTER 1	1	0	0	1	Load counter 1
	0	1	0	1	Read counter 1
COUNTER 2	1	0	1	0	Load counter 2
	0	1	1	0	Read counter 2
MODE WORD or CONTROL WORD	1	0	1	1	Write mode word
--	0	1	1	1	No-operation



# Control Word Register

- This internal register is used to write information to, **prior to using the device.**
- This register is addressed when **A0** and **A1** inputs are logical 1's.
- The data in the register **controls the operation mode** and the selection of either binary or BCD counting format.
- The register can **only** be written to.



# Control Word Format

CONTROL BYTE D7 - D0							
D7	D6	D5	D4	D3	D2	D1	D0
SC1	SC0	RL1	RL0	M2	M1	M0	BCP

D7 SC1	D6 SC0		D5 RL1	D4 RL0	R	D3 M2	D2 M1	D1 M0	M	D0	counts down in	
0	0		0	0	Count	0	0	0	mode 0	0	binary	
0	1				with	0	0	1	mode 1	1	BCD	al count
1	0		0	1	Reload	x	1	0	mode 2		rate generator	
1	1	initial	1	0	Reload	x	1	1	mode 3		square wave generator	
			1	1	Reload	1	0	0	mode 4		software triggered strobe	
					th	1	0	1	mode 5		hardware triggered strobe	

Once a counter is set up, it will remain that way until it is changed by another control word.



# Different uses of the 8253 gate input pin

Signal Status	Low or going low	Rising	High
Mode			
0	Disables counting	--	Enables counting
1	--	1) Initiates counting 2) Resets output after next clock	--
2	1) Disables counting 2) Sets output immediately high	1) Reloads counter 2) Initiates counting	Enables counting
3	1) Disables counting 2) Sets output immediately high	Initiates counting	Enables counting
4	Disables counting	--	Enables counting
5	--	Initiates counting	--

This table shows the different uses of the 8253 gate input pin.

Each mode of operation for the counter has a different use for the GATE input pin.




# Timer Modes - Mode 0

- **Interrupt on Terminal Count**
- The counter will be programmed to an initial value and afterwards **counts down** at a rate equal to the input clock frequency(8 MHz).
- When the count is equal to 0, the **OUT pin** will be a logical 1.
- The output will stay a logical 1 **until the counter is reloaded** with a new value or the same value or **until a mode word is written** to the device.
- Once the counter starts counting down, the **GATE input can disable the internal counting** by setting the GATE to a logical



### Mode 0: Interrupt on Terminal Count

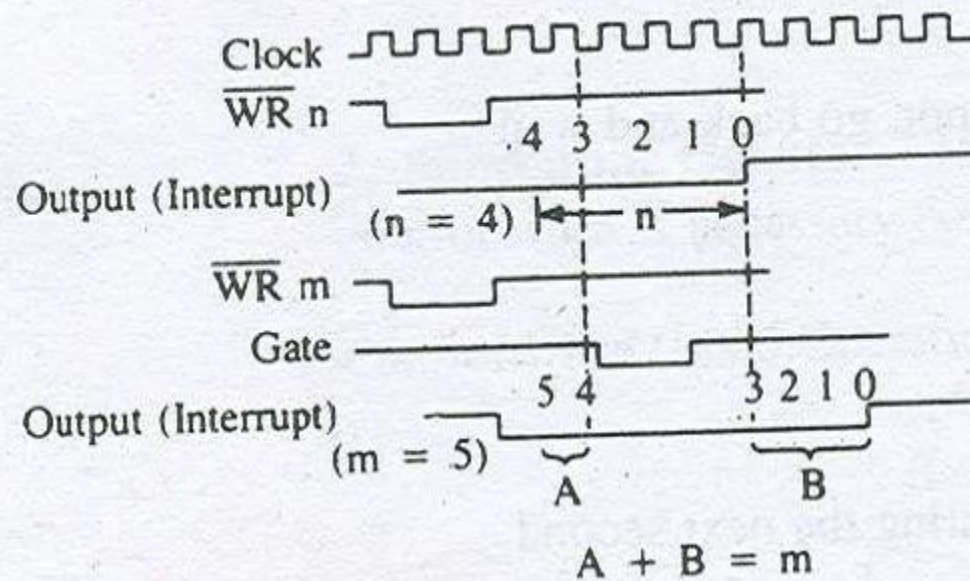


# Timer Modes - Mode 1

- **Programmable One-Shot**
- In mode 1, the device can be setup to give an **output pulse** that is an integer number of clock pulses.
- The one-shot is **triggered** on the rising edge of the GATE input.
- If the trigger occurs during the pulse output, the 8253 will be **retriggered** again.



### Mode 1: Programmable One-Shot

 

# Timer Modes - Mode 2

- **Rate Generator**
- The counter that is programmed for mode 2 becomes a "**divide by n**" counter.
- The **OUT pin** of the counter goes to low for one input clock period.
- The time between the pulses of going low is dependent on the **present count in the counter's register**.






# Timer Modes - Mode 2

- For example, suppose to get an output frequency of **1,000 Hz**, the period would be  **$1 / 1,000 \text{ s} = 1 \text{ ms}$  or  $1,000 \mu\text{s}$** .
- If an input clock of **1 MHz** were applied to the clock input of the counter #0, then the counter #0 would need to be programmed to 1000  $\mu\text{s}$ .
- This could be done in **decimal or in BCD**. (The period of an input clock of 1 MHz is  $1 / 1,000,000 = 1 \mu\text{s}$ .)
- The formula is:  **$n = f_i / f_{out}$** , where  $f_i$  = input clock frequency,  $f_{out}$  = output frequency,  $n$  = value to be loaded.




## Mode 2: Rate Generator Clock

 

# Timer Modes - Mode 3

- **Square Wave Generator**
- Mode 3 is similar to the mode 2 except that the output will be high **for half the period and low for half**.
- **If the count is odd**, the output will be high for  $(n+1)/2$  and low for  $(n-1)/2$  counts.

### Mode 3: Square Wave Generator

 


# Timer Modes - Mode 4

- **Software Triggered Strobe**
- In this mode the programmer can set up the counter to give an **output timeout** starting when the register is loaded.
- **On the terminal count**, when the counter equals to 0, the output will go to a logical 0 for one clock period and then returns to a logical 1.
- Firstly, when the mode is set, the **output will be a logical 1.**



## Mode 4: Software Triggered Strobe

 




# Timer Modes - Mode 5

- **Hardware Triggered Strobe**
- In this mode **the rising edge of the trigger input** will start the counting of the counter.
- The **output goes low for one clock** at the terminal count.
- The counter is **re triggerable**, thus meaning that if the trigger input is taken low and then high during a count sequence, the sequence will start over.
- When the external trigger input goes to a logical 1, **the timer will start to time out.**
- If the **external trigger occurs again**, prior to the time completing a full timeout, the timer will retrigger.



## Mode 5: Hardware Triggered Strobe

 



# Summary

- Pin diagram of 8253
- Architecture
- Control word
- Modes of operation

# Check your understanding

- What are the different modes of operation of timer?

**Thank you**